

[Time: 3 Hours]

[Total Marks: 80]

**Instructions:**

1. Question No: 1 is compulsory.
2. Answer any three from the remaining five questions.

(5 x 4)

1

- a) Explain the working of full wave bridge rectifier circuit with neat waveforms.
- b) Interpret the V-I characteristics of MOSFET.
- c) Draw and explain the frequency response of BJT amplifiers.
- d) Illustrate the working of Schottky diode with its applications.

2

- a) Illustrate with a neat figure, derive the expression of output voltage of subtractor circuit using op-amp. (10)
- b) Draw the hybrid equivalent model of voltage divider bias CE amplifier and derive the expression for voltage gain. (10)

3

- a) Illustrate any three biasing circuits employed in MOSFET amplifiers. (10)
- b) Explain the working of Astable multivibrator using IC555. (10)

4

- a) Illustrate the procedure to find  $I_{CQ}$  and  $V_{CEQ}$  for an emitter bias BJT Amplifier with an example. (10)
- b) Illustrate the working MOSFET CS amplifier. Derive the expression of voltage gain. (10)

5

- a) Explain the construction and working of optoisolators. (10)
- b) Explain the working of op-amp as instrumentation amplifier. (10)

6

Write short notes:

- 1) LED and Zener diodes.
- 2) Inverting and Non-inverting amplifier using op-amp.

(20)

\*\*\*\*\*