

SE · Sem IV (ELEC) (C-Scheme) (Rev-19)

Dec 2025

Duration: 3hrs

Q.P Code 95295

Max Marks: 80

08/12/2025

- Note:
1. Q. No. 1 is compulsory
 2. Attempt any 3 from rest
 3. Make suitable assumptions wherever required
 4. Draw neat and clear diagrams
 5. Write in legible handwriting
 6. Figure to the right indicate full marks

1. Answer any 4 questions 20
 - a. Convert the binary no. 11011.011 in to equivalent decimal, octal and hexadecimal number
 - b. Illustrate the difference between number system and code.
 - c. Convert the T to SR flip flop
 - d. Explain 3bits digital register circuit in brief.
 - e. State the characteristics of the memories and classify the same
 - f. Explain Quantization

2. a. Explain BCD code, excess 3 code and grey code. Tabulate these three code for 4 bits binary number. Explain the concept of negative numbers in binary number system 10
 - b. Explain in detail TTL logic family with example with its advantages and disadvantages 10

3. a. Realize the logical $f(A, B, C, D) = \sum m(0, 1, 3, 4, 5, 7, 9, 11, 12, 13, 14) + d(2, 8, 10)$ using NAND gate after minimizing by K-map 10
 - b. Realize the logic circuit for BCD to excess 3 code converter 10

4. a. Explain the difference between sequential circuit and combinational circuit. Design a logic circuit for three input half adder and full adder. 10
 - b. What is a multiplexer? Explain the construction of basic 8x1 Multiplexer circuit using gates 10

5. a. Explain the working of universal shift register with the help of suitable diagram. 10
 - b. Explain mode 10 synchronous counter with the help of suitable diagrams. 10

6. Write short note on any two 20
 - a. Weighted register Digital to analog converter
 - b. Dual slop method of ADC
 - c. ROM as programmable logic device
 - d. Sample and Hold circuit
