

N. B.

- (1) Question No. 1 is **compulsory**.
- (2) **Attempt** any **three** questions out of remaining questions.
- (3) **Figures** to the **right** indicate **full** marks.
- (4) **Assume** suitable **data** if **necessary**.

- | | | |
|----|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------|
| 1. | Solve any five :- | 20 |
| | a) Draw the bridge used for measurement of low resistance. | |
| | b) Give comparison between digital and analog instruments. | |
| | c) Explain basic working of double frequency meter | |
| | d) Draw the potentiometer used for measuring unknown emf? | |
| | e) Give classification of Transducers with examples of each type | |
| | f) Short note on – resolution and sensitivity of digital meters | |
| 2. | a) Explain Moving iron repulsion type meter and derive the torque equation | 10 |
| | b) Explain the Maxwell’s Bridge. Compare it with bridge Hay’s | 10 |
| 3. | a) A PMMC galvanometer with full scale deflection of 50 mA and coil resistance of 50Ω is to be converted into a multimeter to measure voltage (0-10V) and current (0-5A). Find the suitable values of shunt and multiplier resistance required. | 10 |
| | b) Explain the construction and working of capacitive pressure transducer | 10 |
| 4. | a) Explain with neat sketch transducers used for temperature measurement. Give comparison. | 10 |
| | b) Explain types of error that occur during measurement and means to reduce/avoid them. | 10 |
| 5. | a) Explain instrument transformers and their applications | 10 |
| | b) Explain dual slope type volt meter | 10 |
| 6. | Write a short note on- | |
| | a) Measurement of current using potentiometer | 07 |
| | b) High resistance measurement | 07 |
| | c) Digital energy meter | 06 |