

Time: 3 Hours

[Total Marks-80]

- N.B. 1. Question 1 is compulsory.
 2. Solve any three questions from remaining five.
 3. Assume suitable data if necessary.
 4. Figures to the right indicate full marks.

- Q.1) a. Explain Reciprocity theorem with example. 5
 b. Derive Unit impulse response of RC series circuit. 5
 c. Test whether $P(s) = S^4 + 3S^2 + 5$ is Hurwitz. 5
 d. Derive condition of symmetry for ABCD parameter. 5
- Q.2) a. For oriented graph shown in fig (1), Obtain incidence matrix, fundamental tieset and fundamental cutset matrix. 10

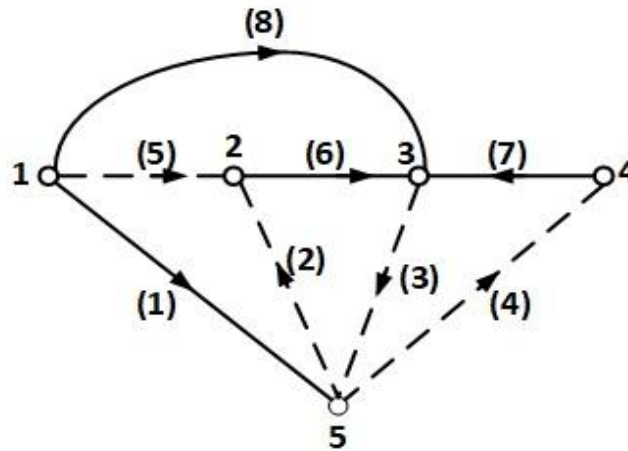


Fig. (1)

- b. For network shown in fig. (2), determine voltage V_1 using Nodal analysis. 10

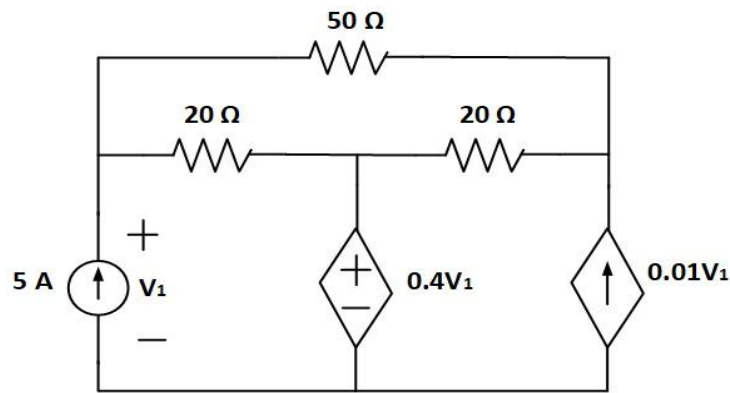


Fig. (2)

- Q.3) a. In network shown in fig. (3), the switch is changed from position 1 to the position 2 at $t=0$, steady state condition having reached before switching. Find the values of i , di/dt and d^2i/dt^2 . 10

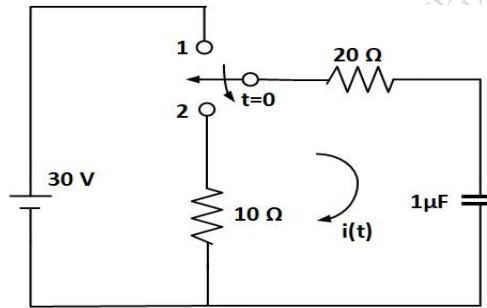


Fig. (3)

- b. In network shown in fig. (4), a steady state condition is achieved with switch open. At $t=0$ switch is closed. Find $V_a(t)$. 10

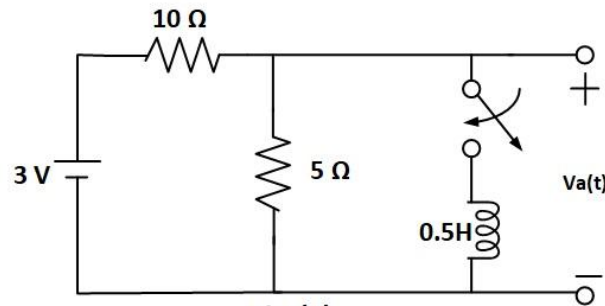


Fig. (4)

- Q. 4) a. In network shown in fig. (5), the switch is moved from a to b at $t=0$. Using Laplace transform method, Determine $i(t)$ and $v(t)$. 10

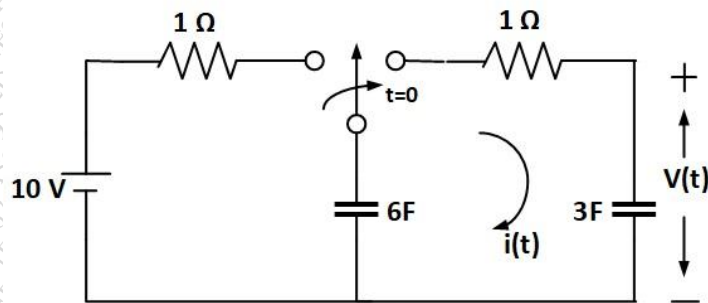


Fig. (5)

- b. Find the value of load impedance Z_L for maximum power transfer in the network shown in fig. (6). Also find value of maximum power. 10

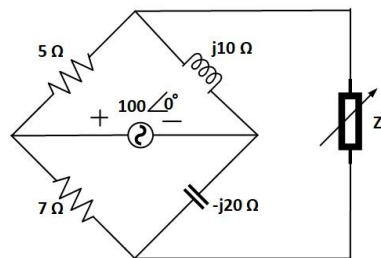


Fig. (6)

- Q. 5) a. Determine voltage transfer function V_2/V_1 for network shown in fig. (7) 10

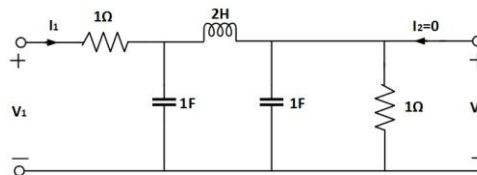


Fig. (7)

- b. The pole zero diagram of the driving point impedance function and network are shown in fig. (8). At DC, the input impedance is resistive and equal to 2 ohm. Determine values of R, L and C. 10

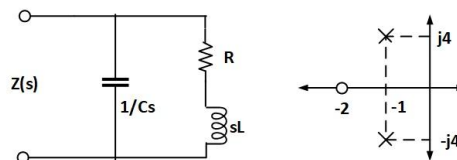


Fig. (8)

- Q. 6) a. Obtain Z and Y parameters for the network shown in fig. (9). 10

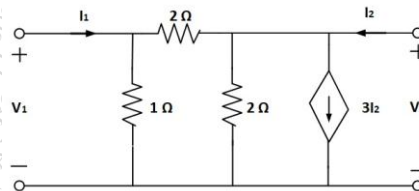


Fig. (9)

- b. Determine the Foster form of realization of the RC impedance function 10

$$Z(s) = \frac{(s + 1)(s + 3)}{s(s + 2)(s + 4)}$$
