

- N.B. : 1. Question **ONE** is **Compulsory**.  
 2. Solve any **THREE** out of remaining.  
 3. **Draw** neat and **clean** Diagrams.  
 4. Assume suitable **data** if required

- Q.1. Attempt the following
- a) Explain the construction of n-channel JFET 5
  - b) List the ideal Characteristics of Op-amp 5
  - c) What is modulation in communication? What is the need for modulation? 5
  - d) Compare TDM and FDM 5
- Q.2. A. Explain Barkhausen Criteria for Oscillation. Calculate the frequency of oscillations of Colpitt's oscillator with  $C_1 = C_2 = 500 \text{ pF}$  and  $L = 1 \text{ mH}$  10  
 B. Derive the equations for  $Z_i, Z_o, A_v$  for common source configuration using voltage divider network 10
- Q.3. A. Explain how op-amp can be used as averaging amplifier in inverting configuration 10  
 B. Explain generation of SSB using phase shift method. 10
- Q.4. A. Explain Superheterodyne receiver in detail and show waveforms at each stage 10  
 B. State and prove Sampling theorem for Low pass Signal. 10
- Q.5. A. Discuss Delta Modulation and Adaptive Delta Modulation 10  
 B. Write short note on TDM-PCM System 10
- Q.6. Write Short note on 10
- a) PLL 10
  - b) Op-amp as Comparator 10

\*\*\*\*\*