

(3 Hours)

[Total Marks: 80]

- N.B. : (1) Question No.1 is compulsory  
(2) Attempt any three from the remaining  
(3) Figures to the right indicate full marks  
(4) Assume suitable data if necessary

- |     |                                                                                                   |    |
|-----|---------------------------------------------------------------------------------------------------|----|
| 1   | Solve any four :-                                                                                 | 20 |
| (a) | List out the advantages of HVDCT                                                                  |    |
| (b) | What is meant by ground return in HVDCT?                                                          |    |
| (c) | Write a short note on Arc back .                                                                  |    |
| (d) | Explain effects of harmonics in HVDC system.                                                      |    |
| (e) | Brief converter transformer.                                                                      |    |
| 2   | (a) Give the equivalent circuit of a 12 pulse converter, What are the different condition modes?  | 10 |
|     | (b) Draw and explain the operation of a 6 pulse converter with overlap angle less than $60^\circ$ | 10 |
| 3   | (a) Explain single commutation failure with diagram and waveform                                  | 10 |
|     | (b) Explain power reversal in HVDCT.                                                              | 10 |
| 4   | (a) Explain over voltage and over currents protection in HVDCT                                    | 10 |
|     | (b) Explain basic control characteristics of HVDCT                                                | 10 |
| 5   | (a) Explain two methods of Equidistant Pulse Control                                              | 10 |
|     | (b) Explain different types of faults in HVDC link.                                               | 10 |
| 6   | (a) Explain the DC filters in HVDCT.                                                              | 10 |
|     | (b) Compare AC transmission and HVDC transmission                                                 | 10 |