

Time : 3 Hours

Total marks : 80

N. B.

- (1) Question No. 1 is **compulsory**.
- (2) **Attempt** any **three** questions out of remaining questions.
- (3) **Figures** to the **right** indicate **full** marks.
- (4) **Assume** suitable **data** if **necessary**.

1. Solve any **four** :-

- a) Show location of different components of HVDC links
  - b) Show the hierarchy in the control of HVDC
  - c) Compare IPC and EPC scheme of firing of HVDC converter bridge
  - d) What is a self-clearing fault in HVDC
  - e) Synthesize the harmonics produced in HVDC converters and name different filters used 20
2. a) For a bridge converter with grid control and overlap less than  $60^\circ$ . Prove that 10
- $$\cos\phi \cong \cos\alpha - \frac{R_c \cdot I_d}{V_{do}}$$
- a) Investigate that single commutation with neat waveforms and diagrams. 10
3. a) Calculate the secondary line voltage of the transformer for a three phase bridge rectifier to provide dc voltage of 120KV. Assume  $\alpha=30^\circ$  and  $\mu=15^\circ$ . What is the effective reactance? When the rectifier gives 800A of dc current. 10
- a) Develop the complete control characteristic of HVDC control from the basic characteristic. 10
4. a) Show the conduction of different valves in HVDC converter for overlap angle  $\mu < 60^\circ$ ,  $\mu = 60^\circ$ ,  $\mu > 60^\circ$ . Also show the number of valves conducting, state which conduction is normal, rare and abnormal. 10
- a) Investigate what happens if current margin is not given and when it is very narrow 10
5. a) Discuss problems related to 'Ground return' 10
- b) Describe 'Power reversal in HVDC' 10
6. a) Evaluate different faults and protections in HVDC 10
- b) Derive equations of fundamental current and rms current drawn by 6-pulse converter and the equation to decide converter transformer rating 10